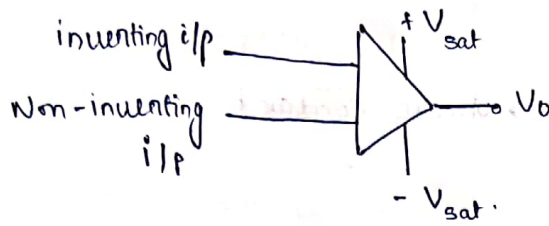


Op - Amp


Circuit Diagram



Pin Diagram of Op-Amp


Op-Amp is an 8 pin IC

Its IC number is 741

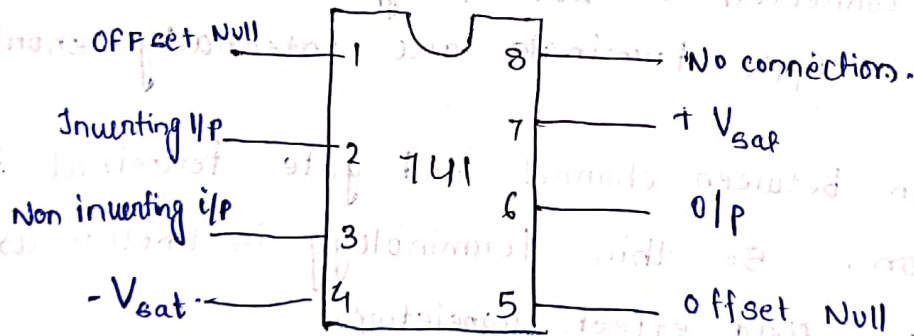


Transfer characteristics of Op-Amp.

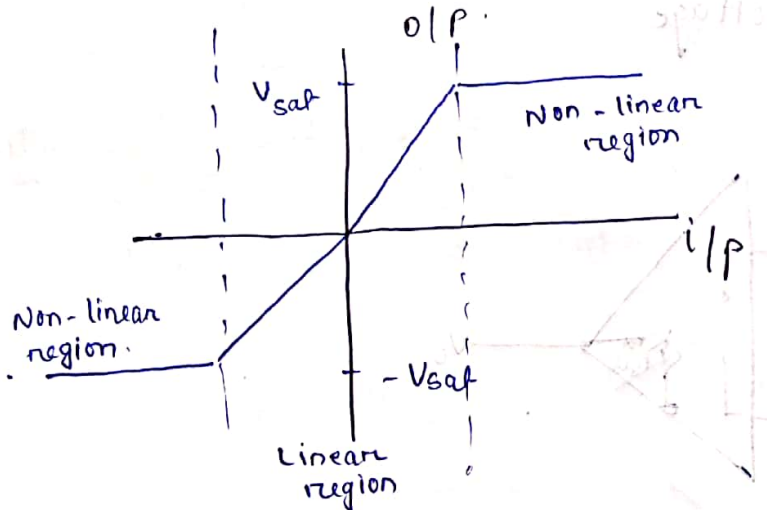It is the characteristics curve between i/p and o/p.



In case of Op-Amp, o/p voltage lies between $-V_{sat}$ to $+V_{sat}$ — $(-V_{sat} \leq V_o \leq +V_{sat})$

Characteristics of Ideal Op-Amp.

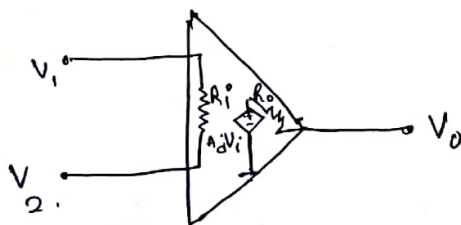

$$V_i = V_1 - V_2$$

R_o = output impedance of Op-Amp

R_i = i/p impedance of Op-Amp

A_d = voltage gain of Op-Amp


V_i = voltage difference between inverting and non-inverting terminal.

1. i/p impedance of ideal Op-Amp is infinite.

2. o/p impedance of Op-Amp is zero.

3. voltage gain of Op-Amp is very high.

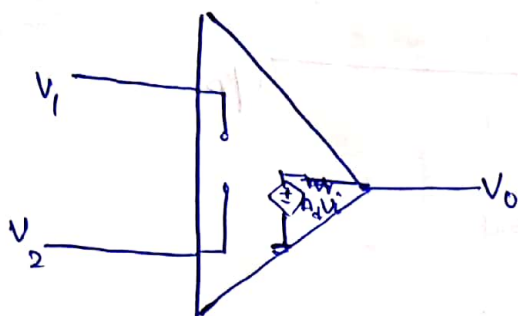5. CMRR (common mode rejection ratio) is infinite.
6. slew rate is very less (i.e. 0)
7. No offset voltage.



* Application of Op-Amp in Linear region.

1. Inverting Amplifier ($-10V \leq V_i \leq 10V$)
2. Non-Inverting Amplifier.
3. Summing Amplifier
4. Differential Amplifier
5. Differentiator &
6. Integrator.

* Virtual Ground :

In case of ground, potential at any point on the ground is 0 volt & potential differential will be 0V & maximum current is going into the ground.


~~In case of ground, potential at any point~~

But in case of virtual ground in op-Amp. Potential at non-inverting terminal is equal to potential at inverting terminal. (~~not vice-versa~~)

Hence p.d between non-inverting and inverting terminal is 0, and no current is flowing between inverting & non-inverting terminal.

Condition for virtual ground in Op-Amp.

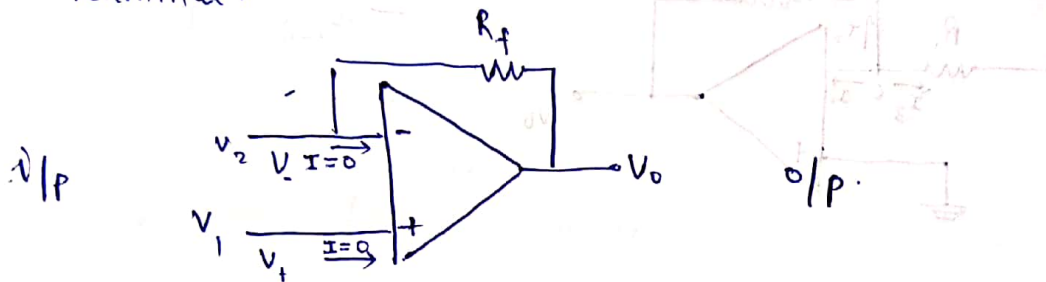
1. There should be a negative feedback from o/p to inverting terminal.



2. Op-Amp should have a very high gain ($A_d \approx 10^6 \approx \infty$)

$$\boxed{\begin{matrix} V_+ = V_- \\ I = 0 \end{matrix}}$$

→ Non-Inverting Op-Amp.

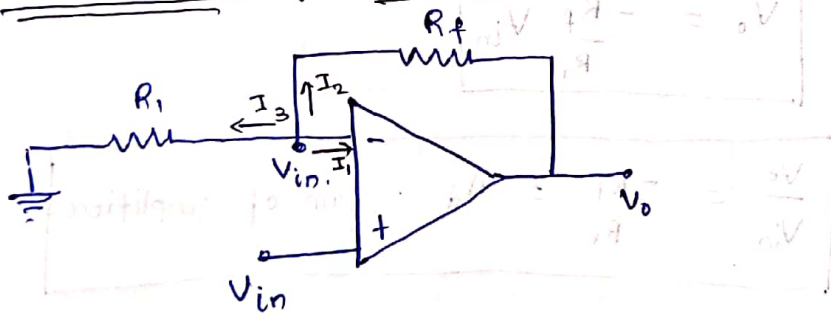

Input is applied at non-inverting terminal of Op-Amp
we have virtual ground present in the Op-Amp.

Applying nodal^{analysis} at inverting terminal.

$$I_1 + I_2 + I_3 = 0$$


$$0 + \frac{V_{in} - V_0}{R_f} + \frac{V_{in} - 0}{R_1} = 0 \Rightarrow$$

$$\boxed{V_0 = \left(1 + \frac{R_f}{R_1}\right) V_{in}}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \left[A_v = \left(1 + \frac{R_f}{R_1} \right) \right] \rightarrow \text{gain of non-inverting amplifier}$$

20/03/2020
80

→ Inverting Amplifier, Op-Amp

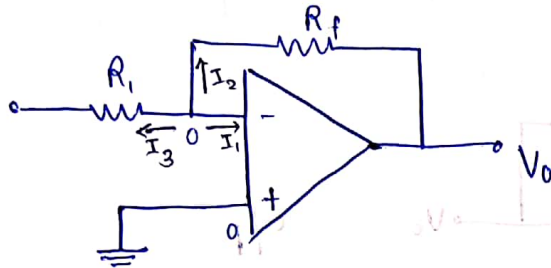

→ In inverting amplifier, the i/p is applied through the ~~non~~ inverting terminal and non-inverting terminal is grounded.

Applying Nodal Equation at inverting terminal,


$$I_1 + I_2 + I_3 = 0.$$

$$\Rightarrow 0 + \frac{0 - V_o}{R_f} + \frac{0 - V_{in}}{R_1} = 0$$

$$\Rightarrow \boxed{V_o = -\frac{R_f}{R_1} V_{in}}$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} = -\frac{R_f}{R_1} = A_d = \text{gain of amplifier}}$$

→ Differential^{CE} Amplifier

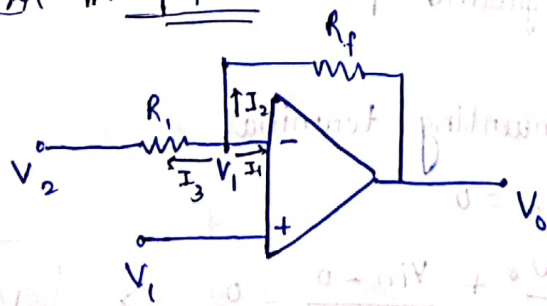

In differential amplifier, the input is applied at both inverting & non inverting terminal.


Applying nodal at inverting terminal,

$$I_1 + I_2 + I_3 = 0$$

$$\Rightarrow 0 + \frac{V_1 - V_0}{R_f} + \frac{V_1 - V_2}{R_1} = 0 \Rightarrow \frac{V_0}{R_f} = \frac{V_1 - V_2}{R_1} + \frac{V_1}{R_f}$$

$$\Rightarrow \boxed{V_0 = R_f \left(\frac{V_1 - V_2}{R_1} + \frac{V_1}{R_f} \right)}$$

→ Summing Amplifier (Adder/Summer)

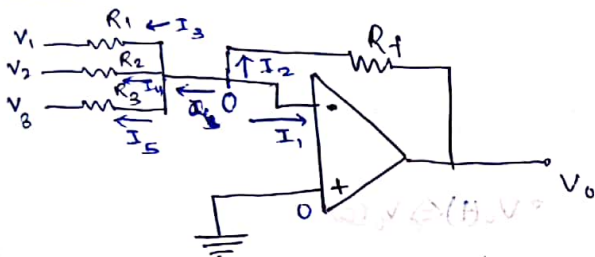

Applying nodal at inverting terminal,

$$I_1 + I_2 + I_3 + I_4 + I_5 = 0$$


$$\Rightarrow 0 + \frac{0 - V_0}{R_f} + \frac{0 - V_1}{R_1} + \frac{0 - V_2}{R_2} + \frac{0 - V_3}{R_3} = 0$$

$$\Rightarrow \boxed{V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)}$$

considering $R_1 = R_2 = R_3 = R_f$,

$$\boxed{V_{01} = -(V_1 + V_2 + V_3)}$$

→ Integrator

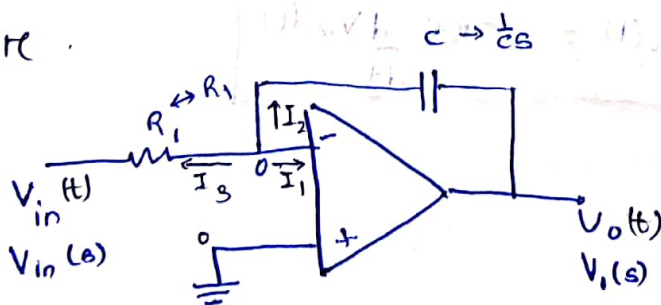

$$C \xrightarrow{L.T} \frac{1}{s}$$

$$L \xrightarrow{L.T} s$$

Note :- $\mathcal{L}\{m(t)\} \rightarrow X(s)$
 $\mathcal{L}\left\{\frac{d}{dt} m(t)\right\} \leftrightarrow sX(s)$
 $\mathcal{L}\left\{\int m(t) dt\right\} \leftrightarrow \frac{X(s)}{s}$


Applying nodal at
 inverting terminal,
 $I_1 + I_2 + I_3 = 0$
 $\Rightarrow 0 + \frac{0 - V_o(s)}{\frac{1}{Cs}} + \frac{0 - V_{in}(s)}{R_1} = 0$

$\Rightarrow V_o(s) = -\frac{1}{RC} \frac{V_{in}(s)}{s}$

By writing converting $V_o(s)$ to t domain,

$V_o(t) = \frac{1}{RC} \int V_{in}(t) dt$

→ Differentiator

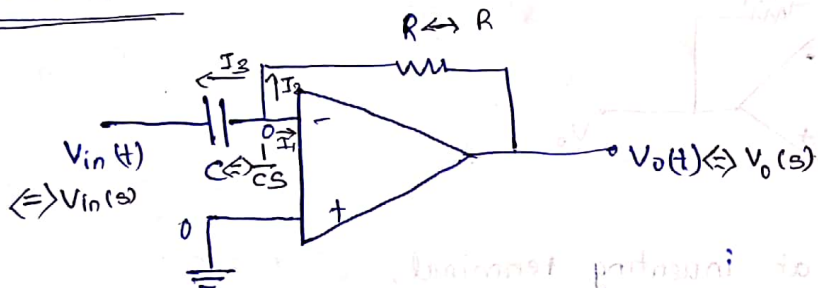

Applying Nodal analysis to inverting terminal


$I_1 + I_2 + I_3 = 0$
 $\Rightarrow 0 + \frac{0 - V_o(s)}{\frac{1}{Cs}} + \frac{0 - V_{in}(s)}{R} = 0$

$\Rightarrow V_o(s) = -RC (s V_{in}(s))$

Converting the signal to t domain

$\Rightarrow V_o(t) = -RC \frac{dV_{in}(t)}{dt}$

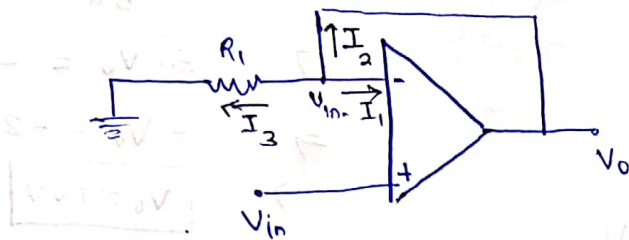→ Buffer or Unit Gain Amplifier or Voltage follower.




$$\Rightarrow V_{in} = V_o \Rightarrow \boxed{V_o = V_{in}}$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} = 1}$$

Numerical Problem Solving

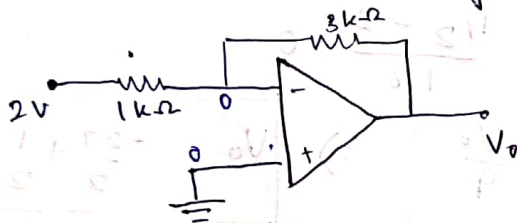1. Determine the output voltage for the following circuits.




Applying nodal at inverting terminal.

$$0 + \frac{0 - V_o}{3k} + \frac{0 - 2}{1k} = 0$$

$$\Rightarrow \frac{-V_o}{3k} = \frac{2}{1k}$$

$$\Rightarrow \boxed{V_o = -6V}$$

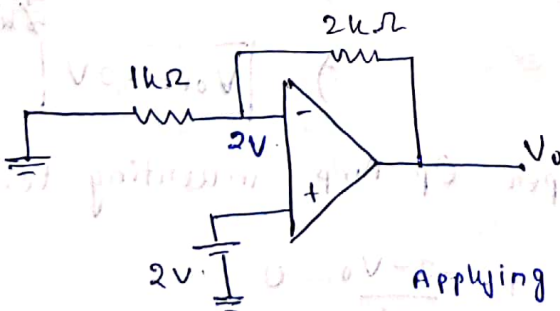


Applying nodal at inverting terminal

$$0 + \frac{2 - 0}{1k} + \frac{2 - V_o}{2k} = 0$$

$$\Rightarrow 2 - V_o = \frac{-2}{1k} \times 2k$$

$$\Rightarrow \boxed{V_o = 6V}$$

Q3

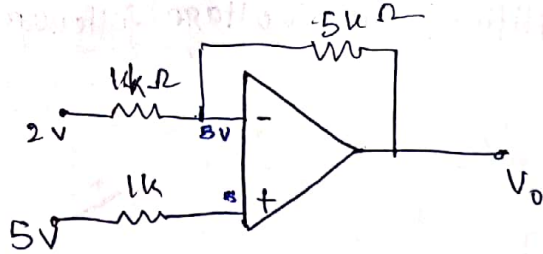

Applying Nodal at inverting terminal.


$$0 + \frac{5 - V_0}{5k} + \frac{5 - 2}{1k} = 0$$

$$\Rightarrow 5 - V_0 = -3 \times 5$$

$$\Rightarrow -V_0 = -20$$

$$\Rightarrow \boxed{V_0 = 20V}$$

Q4

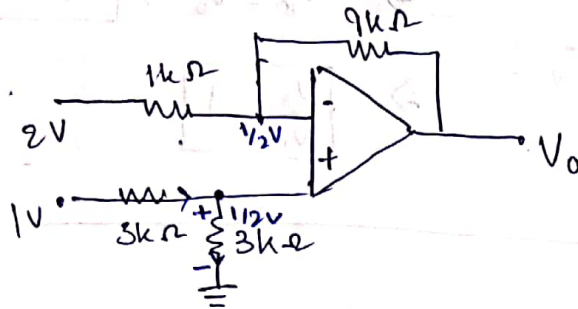


Applying Nodal at inverting terminal.

$$0 + \frac{1/2 - V_0}{9k} + \frac{1/2 - 2}{1k} = 0$$

$$\Rightarrow, -\frac{3}{2} + \frac{1}{18} = \frac{V_0}{9} \Rightarrow \boxed{V_0 = -\frac{27}{2} + \frac{1}{2} = -13V}$$

Q5

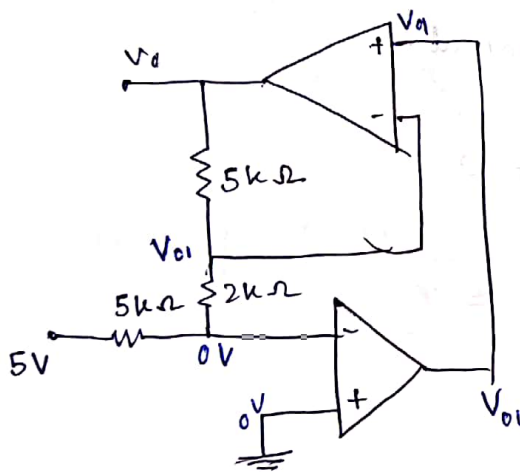

Applying Nodal at lower Op-Amp inverting terminal.

$$0 + \frac{0 - V_{01}}{2k} + \frac{0 - 5}{5k} = 0$$

$$\Rightarrow -V_{01} = \frac{5}{5k} \times 2k$$

$$\Rightarrow \boxed{V_{01} = -2V}$$


Applying Nodal at upper Op-Amp inverting terminal,

$$0 + \frac{-2 - 0}{2k} + \frac{-2 - V_0}{5k} = 0$$

$$\Rightarrow -2 - V_0 = 5$$

$$\Rightarrow \boxed{V_0 = -7V}$$

Determine V_o & I_o for circuit shown.

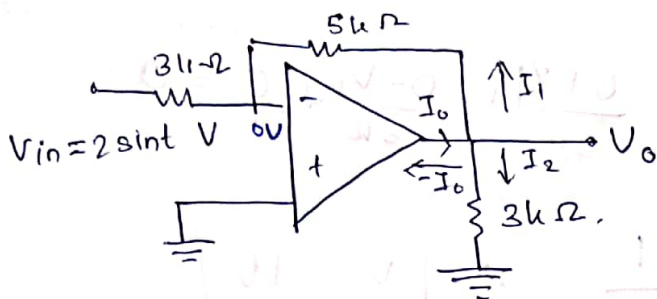

Applying Nodal at inverting terminal,

$$0 + \frac{0 - V_o}{5k} + \frac{0 - 2 \sin t}{3k} = 0$$

$$\Rightarrow V_o = -\frac{10}{3} \sin t V$$

now, $I_o = \frac{V_o}{3k\Omega} = -\frac{10}{9} \sin t \text{ mA}$

Applying Nodal,


$$-I_o + I_1 + I_2 = 0$$

$$\Rightarrow I_o = I_1 + I_2$$

$$= \frac{V_o - 0}{5k} + \frac{V_o - 0}{3k}$$

$$= \frac{8V_o}{15k} = -\frac{8 \times 10^2}{15 \times 3} \sin t \text{ mA} = -\frac{16}{9} \sin t \text{ mA}$$

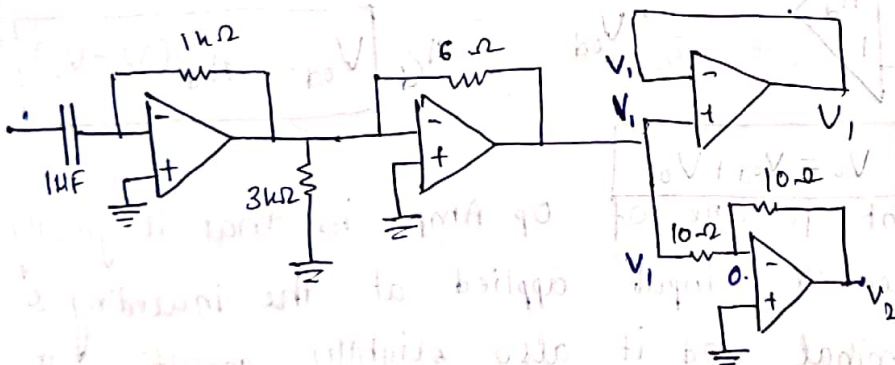Q7. Determine the relation between V_1 & V_2 .




Applying Nodal,

$$\frac{0 - V_1}{10} + \frac{0 - V_2}{10} + 0 = 0$$

$$\Rightarrow \boxed{V_1 = -V_2}$$

Q8

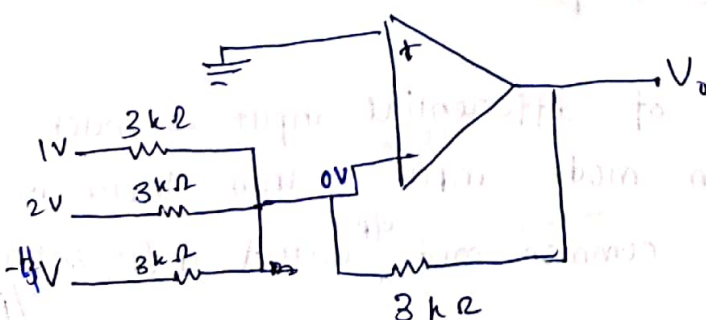


Applying Nodal,

$$\frac{0-1}{3k} + \frac{0-2}{3k} + \frac{0+1}{3k} + \frac{0-V_0}{3k} + 0 = 0$$


$$\Rightarrow \frac{V_0}{3k} = \frac{1}{3k} \Rightarrow \boxed{V_0 = 1V}$$

X ————— X ————— X

Common Mode Rejection Ratio (CMRR)

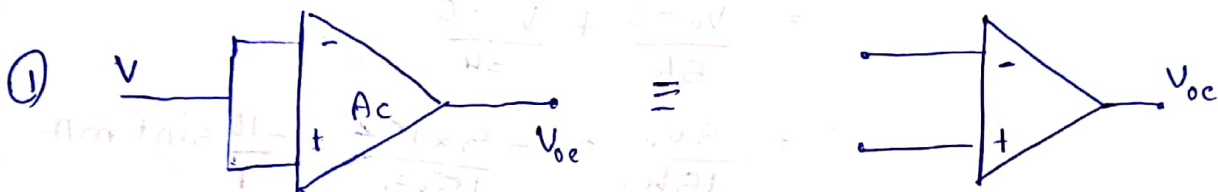

$$\boxed{V_{oc} = A_c \times V}$$

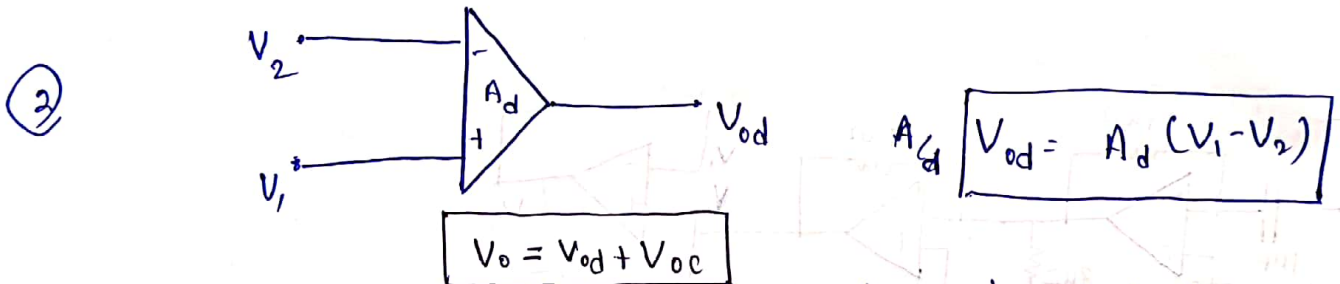

• One of the important feature of Op-Amp is that it greatly amplifies the differential input applied at the inverting & non-inverting terminal and it also slightly amplifies the signal that are both common to both inverting & non inverting terminal.

So, the total output in Op-Amp is due to both differential as well as common mode output.

→ since the amplification of differential input is much greater than common mode input, then there is a chance of rejection of common mode^{o/p} w.r.t differential^{o/p}.

* This rejection is described by a numerical factor which is called CMRR.

* CMRR is defined as the ratio of differential gain to the common mode gain.

$$\boxed{CMRR \triangleq \frac{A_d}{A_c}}$$

A_d = Differential Gain

A_c = Common mode gain

* Power Gain in Absolute Scale.

$$\boxed{A_p = \frac{P_o}{P_{in}}}$$

* Power Gain in Logarithmic Scale. (dB)

$$\boxed{A_p|_{dB} = 10 \log_{10} \frac{P_o}{P_{in}}}$$

* Voltage Gain.

$$A_v = \frac{V_o}{V_{in}} \rightarrow \text{Absolute Scale}$$

$$A_v|_{dB} = 20 \log_{10} \left(\frac{V_o}{V_{in}} \right) \text{ dB} \rightarrow \text{dB scale}$$

$$A_i = \frac{I_o}{I_{in}} \rightarrow \text{Absolute Scale}$$

$$A_i|_{dB} = 20 \log_{10} \left(\frac{I_o}{I_{in}} \right) \text{ dB} \rightarrow \text{dB scale}$$

$$CMRR = \frac{A_d}{A_c} \rightarrow \text{Absolute Scale} \quad \bullet \quad CMRR = 20 \log_{10} \left(\frac{A_d}{A_c} \right) \text{ dB} \rightarrow \text{dB scale}$$

Q In an Op-Amp with $A_d = 10^6$ & CMRR is 20dB, what is the ~~cm~~ A_c ?

Ans:

~~$$20 = 20 \log_{10} \left(\frac{10^6}{A_c} \right) \text{ dB} \rightarrow$$~~

$$CMRR = \frac{A_d}{A_c} \Rightarrow CMRR = \frac{10^6}{A_c}$$
$$CMRR|_{dB} = 20 \log_{10} \left(\frac{A_d}{A_c} \right) \text{ dB}$$

$$\Rightarrow 20 = 20 \log_{10} \text{CMRR}$$

$$\Rightarrow \boxed{10^1 = \text{CMRR}}$$

$$\Rightarrow 10 = \frac{10^6}{A_c} \Rightarrow \boxed{A_c = 10^5}$$

Q Repeat the above question with $A_d = 20\text{dB}$ and determine the value of A_c .

$$\text{CMRR}_{\text{dB}} = 20 \log_{10} \left(\frac{A_d}{A_c} \right)$$


$$\Rightarrow 120 = 20 \log 20 - \log A_c$$

$$\Rightarrow 1 - \log 20 = -\log A_c$$

$$\Rightarrow \log 2 = \log A_c \Rightarrow \boxed{A_c = 2}$$

06/04/2020

Continuation of CMRR

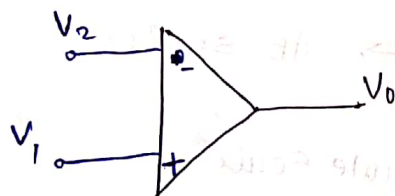

$$\begin{aligned} V_0 &= V_{oc} + V_{od} \\ &= A_c \cdot V_c + A_d \cdot V_d \end{aligned}$$

\downarrow common mode gain \downarrow diff. mode gain

$$V_c = \text{Common mode i/p} = \frac{V_1 + V_2}{2}$$

$$V_d = \text{Diff. mode i/p} = V_1 - V_2$$

$$V_0 = A_c \left(\frac{V_1 + V_2}{2} \right) + A_d (V_1 - V_2)$$


$$= \left(\frac{A_c + A_d}{2} \right) V_1 + \left(\frac{A_c - A_d}{2} \right) V_2$$

$$= A_1 V_1 + A_2 V_2$$


where $A_1 = A_d + \frac{A_c}{2}$

$A_2 = \frac{A_c}{2} - A_d$


$$A_1 = \left. \frac{V_o}{V_1} \right|_{V_2=0}$$

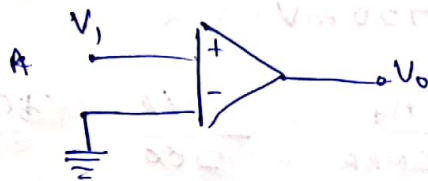

$$A_2 = \left. \frac{V_o}{V_2} \right|_{V_1=0}$$

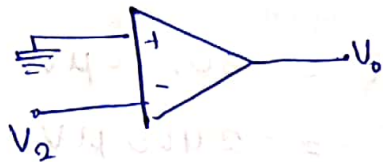

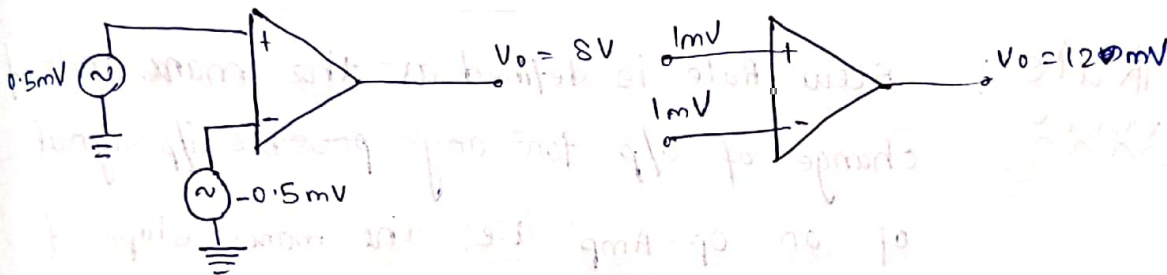Calculate CMRR for the setup shown below.



$$V_{od} = 8V$$

$$V_{oc} = 12mV$$

$$V_o = V_{oc} + V_{od} = 8V + 12mV$$

$$V_{oc} = A_c V_c = A_c \times \frac{V_1 + V_2}{2} \Rightarrow 12mV = A_c \times 1mV$$

$$V_{od} = A_d V_d = A_d (V_1 - V_2) = A_d (0.5 - (-0.5))mV$$

$$\Rightarrow 8V = A_d \times 1mV \Rightarrow A_d = 8000$$

$$CMRR = \frac{A_d}{A_c} = \frac{8000}{12} \Rightarrow \text{Absolute Scale}$$

$$CMRR|_{dB} = 20 \log_{10} \left(\frac{8000}{12} \right) dB \Rightarrow \text{Logarithmic Scale.}$$

Ex: $V_{i1} = 20\mu V$ $V_{i2} = 140\mu V$ $A_d = 6000$ $CMRR = 200$
determine the output voltage.

Sol: $V_o = V_{oc} + V_{od}$
 $= A_d V_d + A_c V_c$
 $\Rightarrow V_d = -120\mu V$ $V_c = 80\mu V$

$$V_{od} = A_d \cdot V_d = -120 \text{ MV} \times 6000 \\ = -720 \text{ mV}$$

$$A_c = \frac{A_d}{\text{CMRR}} = \frac{6000}{200} = 30$$

$$\text{now, } V_{oc} = A_c \cdot V_c = 30 \cdot 80 \mu\text{V} \\ = 2400 \mu\text{V} = 2.4 \text{ mV}$$

$$\text{so, } V_o = (-720 + 2.4) \text{ mV} = -717.6 \text{ mV}$$

* Slew Rate: Slew Rate is defined as the max rate of change of o/p for any possible i/p signal of an Op-Amp. i.e. the max. slope of o/p of Op-Amp.


$$\text{Slew Rate} = \left. \frac{dV_o}{dt} \right|_{\text{max.}} \quad \boxed{V/\mu\text{s} = \text{Unit}}$$

Q For an Op-Amp, $V_o = V_m \sin 2\pi f_m t$. Determine the slew rate of the Op-Amp

$$\text{Slew rate} = \left. \frac{dV_o}{dt} \right|_{\text{max}} = V_m \frac{d \sin 2\pi f_m t}{dt} \\ = 2\pi V_m f_m \cos 2\pi f_m t \bigg|_{\text{max}}$$

$$\boxed{\text{S.R} = 2\pi f_m V_m, V/\mu\text{s}}$$

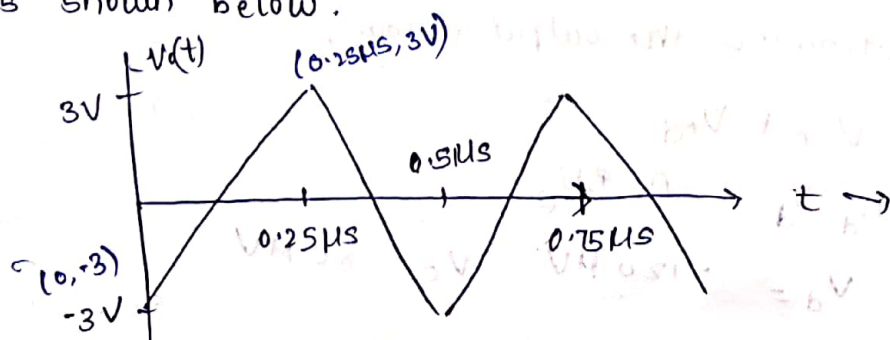Q Determine the slew Rate of the given o/p of the op-Amp which is shown below.



$$S.R = \left. \frac{dV_o}{dt} \right|_{\text{max}} = \frac{[3 - (-3)] V}{0.25 \text{ MS}} = \frac{6 V}{0.25 \text{ MS}} = 24 \text{ V/MS}$$

Block Diagram of Op-Amp

